DDR2 Application Note

ODT(On Die Termination) Control

March 2006


Product Planning & Application Engineering Team MEMORY DIVISION SAMSUNG ELECTRONICS Co., LTD

Product Planning & Application Eng. Team



DDR2 ODT (On Die Termination)

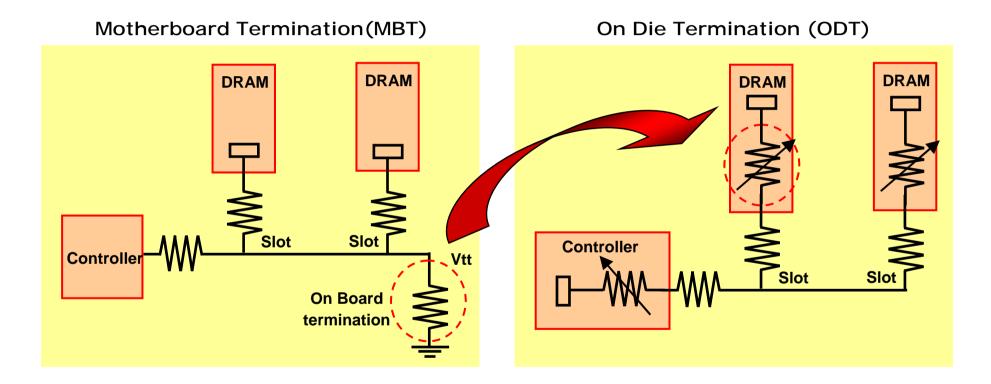
□ On board termination resistance is integrated inside of DRAM





On Die Termination On/Off Control

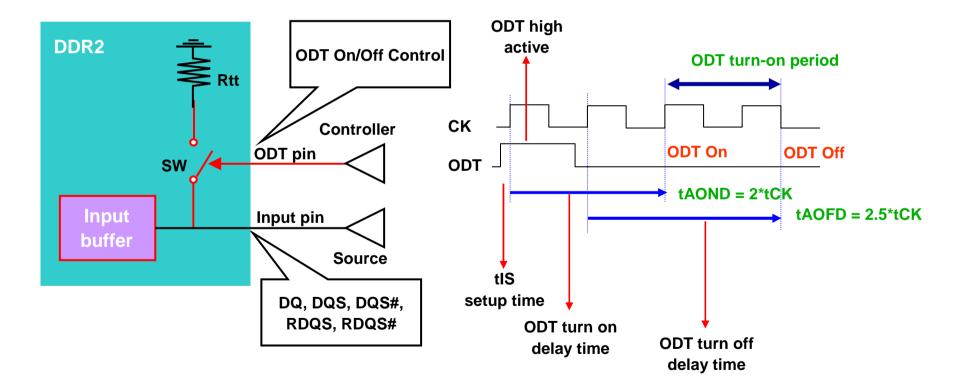- ODT turn on/off is controlled by ODT pin
- □ One ODT control pin per DRAM : Turn-on or Turn-off control
- Two ODT control pin per DIMM to support rank by rank control But in most application, one ODT pin per slot is being used




Product Planning & Application Eng. Team



On Die Termination Value Selection

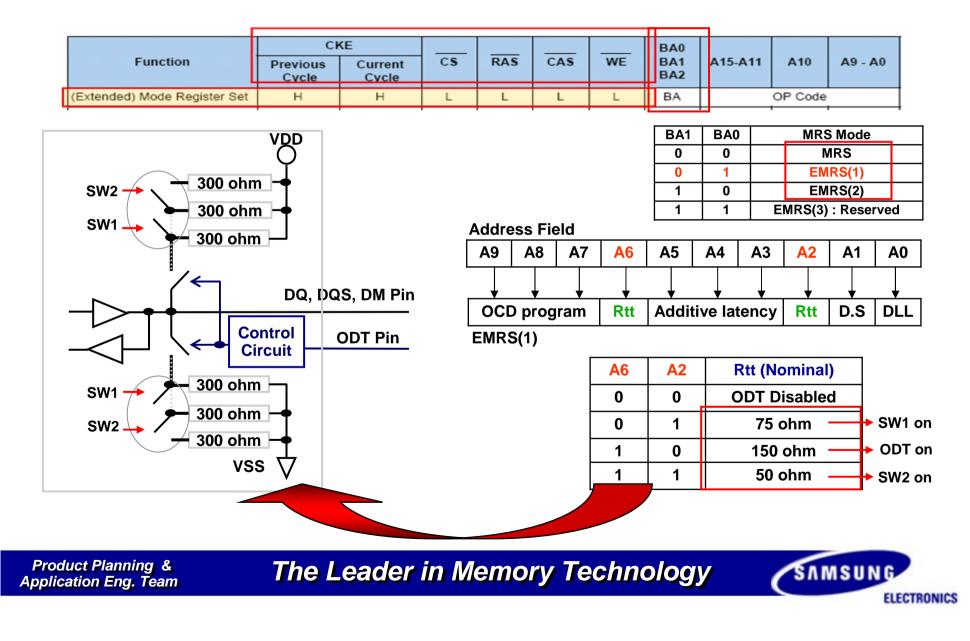□ ODT value should be determined during power-up by EMRS



Test Condition for ODT Verification


□ Capacitance Specification for DDR2-667 & 800

Parameter	DDR2-667/DDR2-800		UNIT	
Parameter	MIN	MAX		
Input capacitance CK, /CK	1.0	2.0	pF	
Input capacitance Delta, CK, /CK	-	0.25	pF	
Input capacitance C/A	1.0	2.0	pF	
Input capacitance Delta, C/A	-	0.25	pF	
Input capacitance DQ/DM/DQS	2.5	3.5	pF	
Input capacitance Delta, DQ/DM/DQS	-	0.5	pF	



ODT Case Study @DDR2-667 Writes

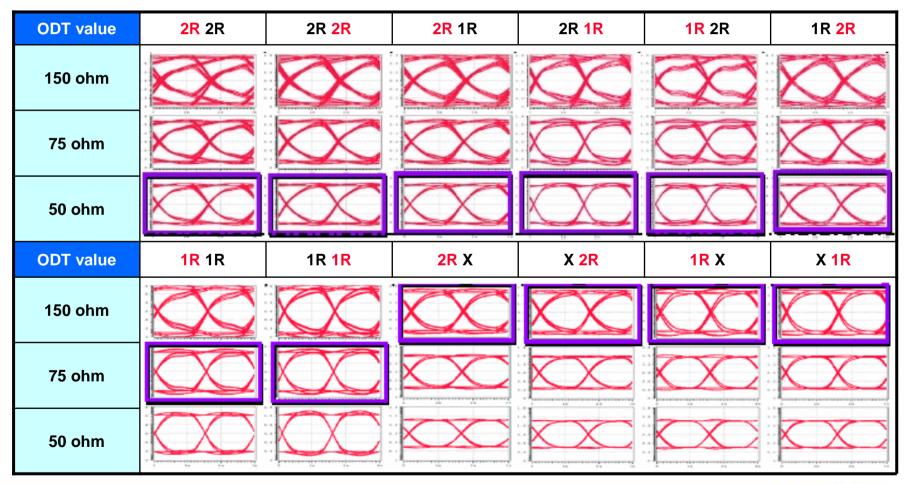- Application Note
- For two slot population, 50ohm seems to be better than 75ohm in term of signal integrity
- □ For one slot population, even 150ohm seems O.K.




Product Planning & Application Eng. Team



ODT Case Study @DDR2-800 Writes

For two slot population, 50ohm seems to be better than 75ohm in term of signal integrity

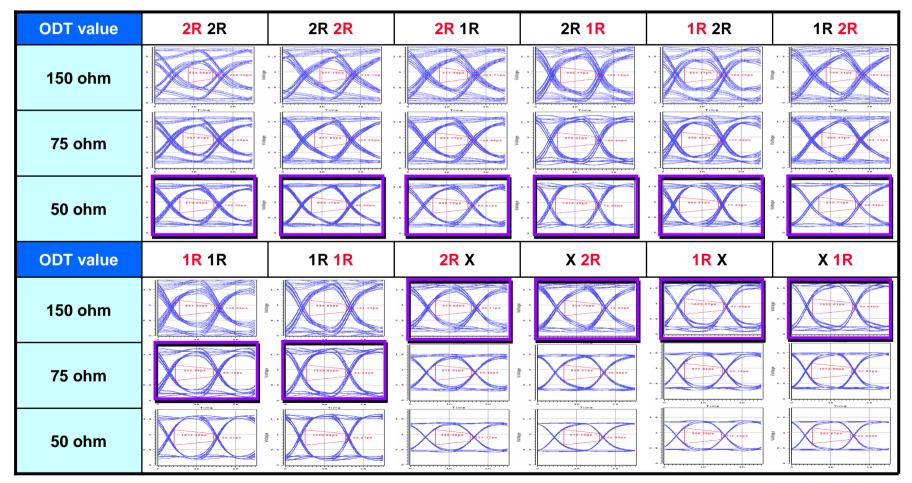□ For one slot population, even 150ohm seems O.K.



Product Planning & Application Eng. Team The Leader in Memory Technology




Application

Note

Termination Matrix for Writes to DRAM


Configuration	10/+:4-0	Target DQ ODT Resistance RTT				
	Write To	Controller	Module in slot 1		Module in slot 2	
			Rank 1	Rank 2	Rank 1	Rank 2
2R 2R	slot 1	Infinite	Infinite	Infinite	75 or 50 ohm	Infinite
	slot 2	Infinite	75 or 50 ohm	Infinite	Infinite	Infinite
2R 1R	slot 1	Infinite	Infinite	Infinite	75 or 50 ohm	Unpopulated
	slot 2	Infinite	75 or 50 ohm	Infinite	Infinite	Unpopulated
1R 2R	slot 1	Infinite	Infinite	Unpopulated	75 or 50 ohm	Infinite
	slot 2	Infinite	75 or 50 ohm	Unpopulated	Infinite	Infinite
1R 1R	slot 1	Infinite	Infinite	Unpopulated	75 or 50 ohm	Unpopulated
	slot 2	Infinite	75 or 50 ohm	Unpopulated	Infinite	Unpopulated
2R Empty	slot 1	Infinite	150 ohm	Infinite	Unpopulated	Unpopulated
Empty 2R	slot 2	Infinite	Unpopulated	Unpopulated	150 ohm	Infinite
1R Empty	slot 1	Infinite	150 ohm	Unpopulated	Unpopulated	Unpopulated
Empty 1R	slot 2	Infinite	Unpopulated	Unpopulated	150 ohm	Unpopulated

ODT on a controller always turned-off

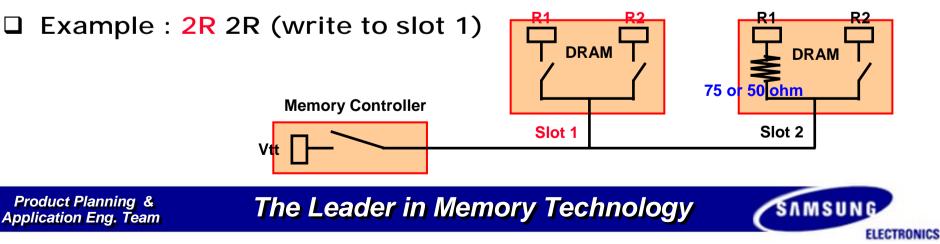

ODT Case Study @DDR2-667 Reads

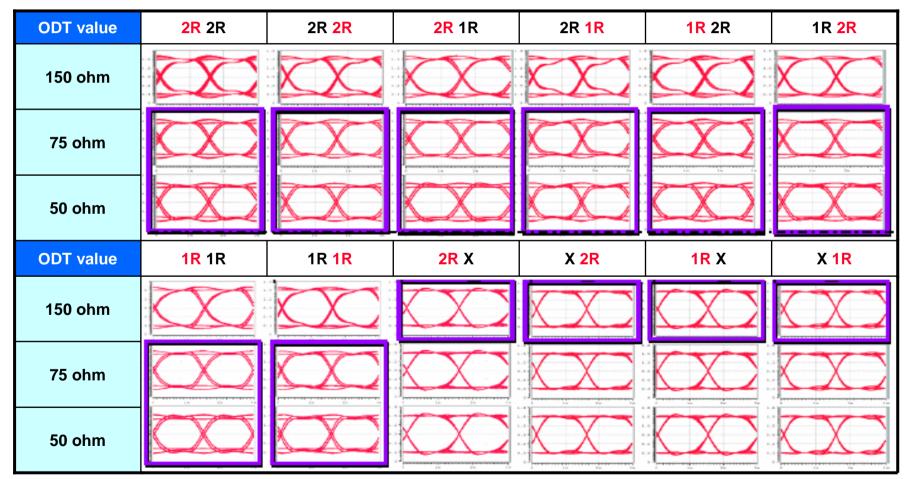- □ For two slot population, either 750hm or 500hm could be O.K. → 500hm does not help on reads that much
- □ For one slot population, even 150ohm seems O.K.



Product Planning & Application Eng. Team

The Leader in Memory Technology




Application

Note

ODT Case Study @DDR2-800 Reads

□ For two slot population, either 750hm or 500hm could be 0.K. → 500hm does not help on reads that much

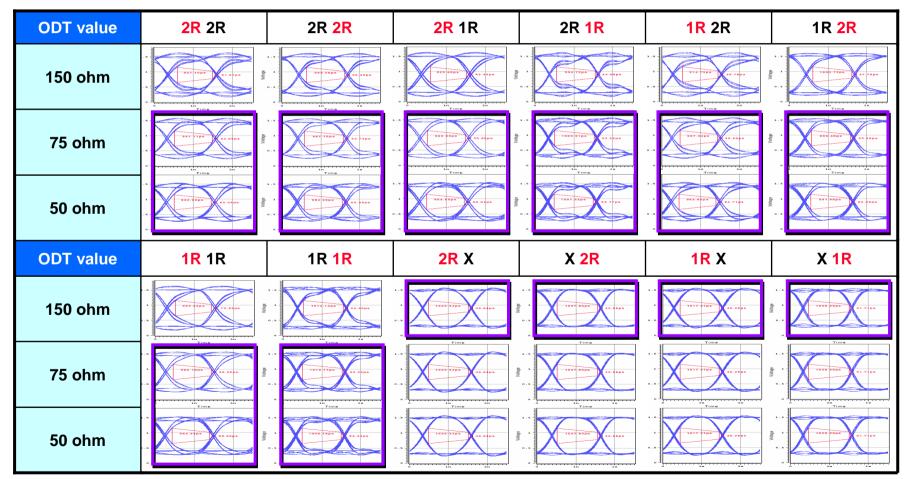□ For one slot population, even 150ohm seems O.K.



Product Planning & Application Eng. Team The Leader in Memory Technology




Application

Note

Termination Matrix for Reads to DRAM

Configuration	Deed	Target DQ ODT Resistance RTT				
	Read from	Controller	Module in slot 1		Module in slot 2	
			Rank 1	Rank 2	Rank 1	Rank 2
2R 2R	slot 1	150 ohm	Infinite	Infinite	75 or 50 ohm	Infinite
	slot 2	150 ohm	75 or 50 ohm	Infinite	Infinite	Infinite
2R 1R	slot 1	150 ohm	Infinite	Infinite	75 or 50 ohm	Unpopulated
	slot 2	150 ohm	75 or 50 ohm	Infinite	Infinite	Unpopulated
1R 2R	slot 1	150 ohm	Infinite	Unpopulated	75 or 50 ohm	Infinite
	slot 2	150 ohm	75 or 50 ohm	Unpopulated	Infinite	Infinite
1R 1R	slot 1	150 ohm	Infinite	Unpopulated	75 or 50 ohm	Unpopulated
	slot 2	150 ohm	75 or 50 ohm	Unpopulated	Infinite	Unpopulated
2R Empty	slot 1	75 ohm	Infinite	Infinite	Unpopulated	Unpopulated
Empty 2R	slot 2	75 ohm	Unpopulated	Unpopulated	Infinite	Infinite
1R Empty	slot 1	75 ohm	Infinite	Unpopulated	Unpopulated	Unpopulated
Empty 1R	slot 2	75 ohm	Unpopulated	Unpopulated	Infinite	Unpopulated

□ ODT on a controller always turned-on

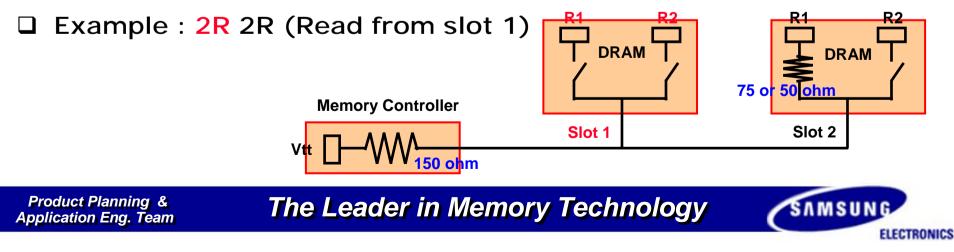

Summary of ODT Control

Servironment and set during initialization sequence

- ✓ For one slot/channel implementation, 150ohm seems O.K.
- For two slots/channel implementation, ODT value need to be determined properly
- ✓ For DDR2-400/533, 75ohm seems O.K.
- ✓ For DDR2-667/800, 500hm is better than 750hm

IFF ODT trun-on/off is controlled by ODT pin

- There're more possible termination methods, but not covered in this material
 - For example, 37.5ohm termination is possible with both ODTs turned-on on a dual rank DIMM, which may result "better signal integrity, but relatively small voltage swing and more power consumption."

