

---


Solutions to Problems Marked with a \* in  
Logic and Computer Design Fundamentals, 4th Edition  
**Chapter 3**

---


© 2008 Pearson Education, Inc.


---

**3-2.\***

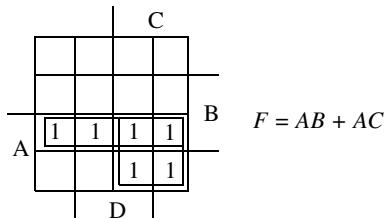

**3-24.\***

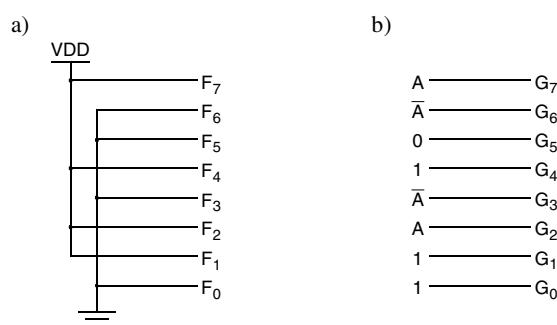

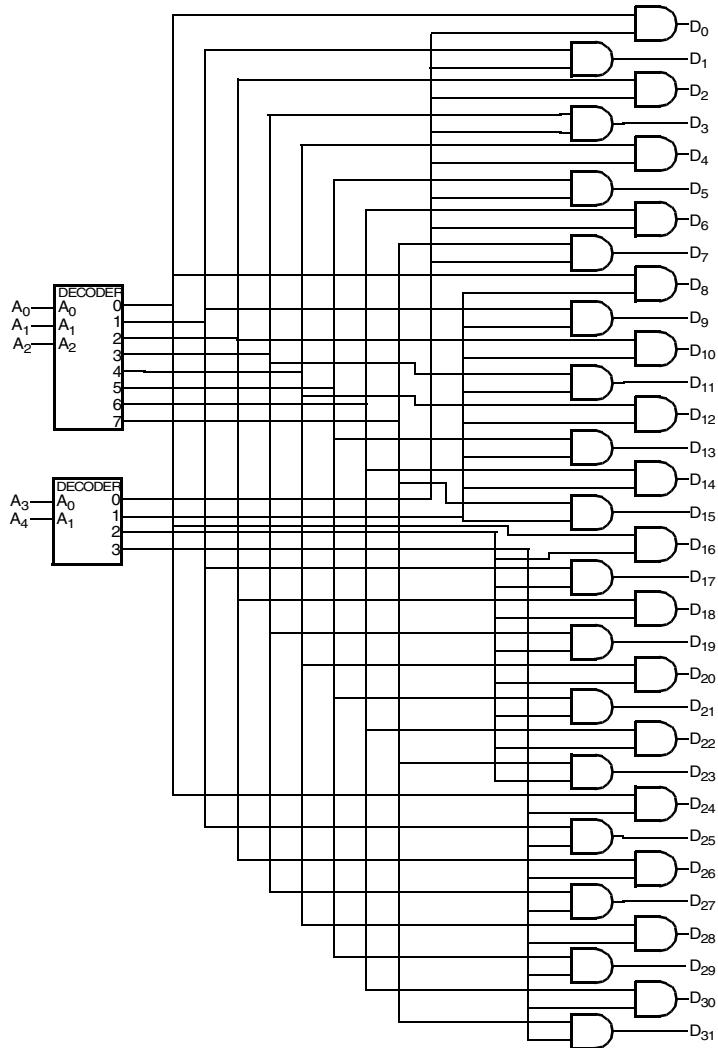
3-30.\*  

 3-35.\*  


$D_3$	$D_2$	$D_1$	$D_0$	$A_1$	$A_0$	$V$
0	0	0	0	X	X	0
X	X	X	1	0	0	1
X	X	1	0	0	1	1
X	1	0	0	1	0	1
1	0	0	0	1	1	1

$$V = D_0 + D_1 + D_2 + D_3$$

$$A_0 = \overline{D}_0(D_1 + \overline{D}_2)$$
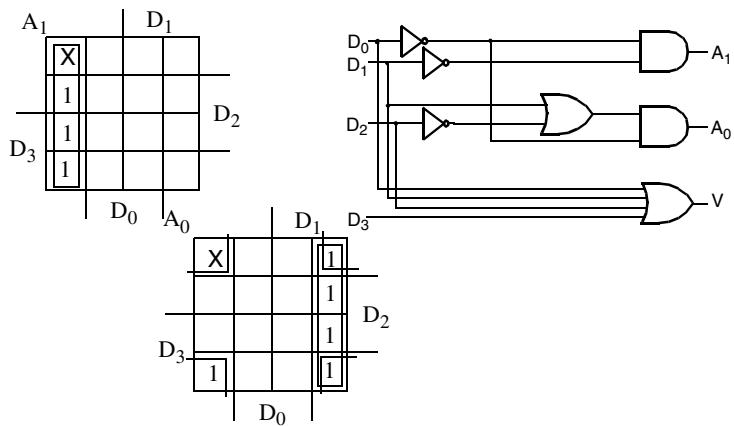
$$A_1 = \overline{D}_0\overline{D}_1$$

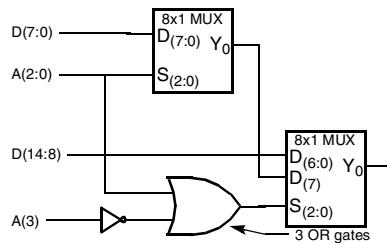

**3-42.\***

**3-43.\***

A <sub>1</sub>	A <sub>0</sub>	E	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>
0	0	0	0	0	0	0
0	0	1	1	0	0	0
0	1	0	0	0	0	0
0	1	1	0	1	0	0
1	0	0	0	0	0	0
1	0	1	0	0	1	0
1	1	0	0	0	0	0
1	1	1	0	0	0	1

Consider E as the data input and A<sub>0</sub>, A<sub>1</sub> as the select lines. For a given combination on (A<sub>1</sub>, A<sub>0</sub>), the value of E is distributed to the corresponding D output. For example for (A<sub>1</sub>, A<sub>0</sub>) = (10), the value of E appears on D<sub>2</sub>, while all other outputs have value 0.

**3-47.\***

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

