

**Solutions to Problems Marked with a * in
Logic and Computer Design Fundamentals, 4th Edition**
Chapter 9

© 2008 Pearson Education, Inc.

9-2.*

$$C = C_8$$

$$V = C_8 \oplus C_7$$


$$Z = \overline{F_7 + F_6 + F_5 + F_4 + F_3 + F_2 + F_1 + F_0}$$

$$N = F_7$$

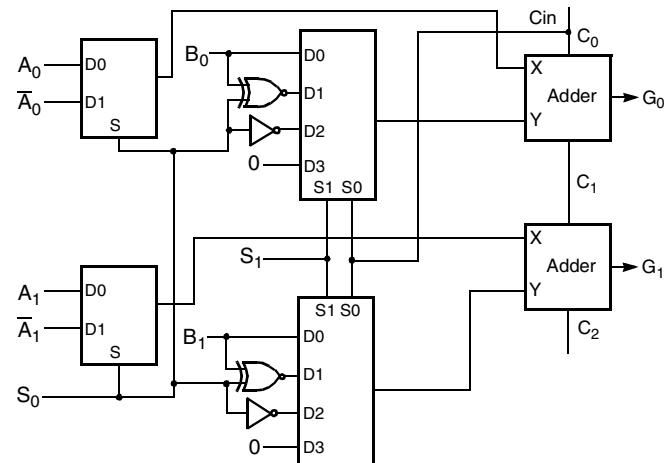
9-3.*

$$X = S_0 \bar{A} + \bar{S}_0 A$$

$$Y = \bar{S}_1 \bar{C}_{in} B + \bar{S}_1 S_0 B + \bar{S}_1 \bar{S}_0 \bar{B} + S_1 \bar{S}_0 \bar{C}_{in}$$



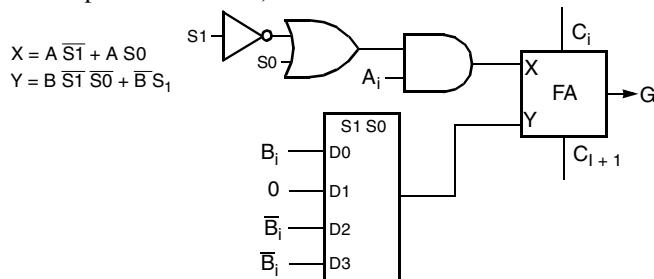9-4.* (Errata: Delete “1” after problem number)



9-6.*

- a) XOR = 00, NAND = 01, NOR = 10 XNOR = 11
 $\text{Out} = S_1 \bar{A} \bar{B} + \bar{S}_1 \bar{A} B + \bar{S}_1 A \bar{B} + S_1 S_0 AB + (\text{one of } S_0 \bar{A} \bar{B} + \bar{S}_1 S_0 \bar{A})$
 b) The above is a simplest result.

9-8.*

- (a) 1010 (b) 1110 (c) 0101 (d) 1101

9-10.*

- | | | | |
|--|-------------------|---------------------------------------|-------------------|
| (a) $R5 \leftarrow R4 \wedge R5$ | $R5 = 0000\ 0100$ | (d) $R5 \leftarrow R0$ | $R5 = 0000\ 0000$ |
| (b) $R6 \leftarrow R2 + \overline{R4} + 1$ | $R6 = 1111\ 1110$ | (e) $R4 \leftarrow sr\text{Constant}$ | $R4 = 0000\ 0011$ |
| (c) $R5 \leftarrow R0$ | $R5 = 0000\ 0000$ | (f) $R3 \leftarrow \text{Data in}$ | $R3 = 0001\ 1011$ |

9-13.*

- a) Opcode = 8 bits b) 18 bits c) 262,144 d) +131,071 and -131,072