 


Solutions to Problems Marked with a * in
 Logic and Computer Design Fundamentals, 4th Edition
Chapter 5

© 2008 Pearson Education, Inc.

5-7.*

Present state			Input	Next state		
A	B	C	X	A	B	C
0	0	0	0	1	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	1	1	0
0	1	1	0	1	0	1
0	1	1	1	0	0	1
1	0	0	0	1	1	0
1	0	0	1	0	1	0
1	0	1	0	0	1	0
1	0	1	1	1	1	0
1	1	0	0	0	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	0	1	1




State diagram is the combination of the above two diagrams.

5-11.*

$$S_A = B \quad S_B = \overline{X \oplus A}$$

$$R_A = \overline{B} \quad R_B = X \oplus A$$


Present state			Input	Next state		Output
A	B	X	A	B	Y	
0	0	0	0	1	0	
0	0	1	0	0	1	
0	1	0	1	1	1	
0	1	1	1	0	0	
1	0	0	0	0	1	
1	0	1	0	1	0	
1	1	0	1	0	0	
1	1	1	1	1	1	

 

Format: X/Y

5-13.*

Present state		Input	Next state	
A	B	X	A	B
0	0	0	0	0
0	0	1	1	0
0	1	0	0	1
0	1	1	0	0
1	0	0	1	0
1	0	1	1	1
1	1	0	1	1
1	1	1	0	1

 


Logic diagram not given.

Problem Solutions – Chapter 5

5-18.*

Format: XY/Z (x = unspecified)

 

Present state	Inputs		Next state	Output
$Q(t)$	X	Y	$Q(t+1)$	Z
0	0	0	0	0
0	0	1	0	X
0	1	0	1	1
0	1	1	0	X
1	0	0	1	1
1	0	1	0	X
1	1	0	1	0
1	1	1	0	X

5-26.*

To use a one-hot assignment, the two flip-flops A and B need to be replaced with four flip-flops Y4, Y3, Y2, Y1.

No Reset State Specified.


Present State		Input				Next State				Output			
A	B	$Y4$	$Y3$	$Y2$	$Y1$	X	A'	B''	$Y4'$	$Y3'$	$Y2'$	$Y1'$	Z
0	0	0	0	0	1	0	0	1	0	0	1	0	1
0	0	0	0	0	1	1	0	0	0	0	0	1	1
0	1	0	0	1	0	0	0	1	0	0	1	0	0
0	1	0	0	1	0	1	1	0	0	1	0	0	0
1	0	0	1	0	0	0	1	1	1	0	0	0	0
1	0	0	1	0	0	1	1	0	0	1	0	0	0
1	1	1	0	0	0	0	1	1	1	0	0	0	0
1	1	1	0	0	0	1	0	0	0	0	0	1	0

$$D1 = Y1' = X \cdot Y1 + X \cdot Y4$$

$$D2 = Y2' = \bar{X} \cdot Y1 + \bar{X} \cdot Y2$$

$$D3 = Y3' = X \cdot Y2 + X \cdot Y3$$
 
$$D4 = Y4' = \bar{X} \cdot Y3 + \bar{X} \cdot Y4$$




Problem Solutions – Chapter 5

5-27.*

a)

S	R	Q	
0	0	Q	No Change
0	1	0	Reset
1	0	1	Set
1	1	1	Set

 


c)


Present state	Input		Next state			
	Q	S	R	Q(t+1)	A	B
0	0	0	0	0	0	x
0	0	0	1	0	0	x
0	0	1	0	1	1	0
0	0	1	1	1	1	0
1	1	0	0	1	x	0
1	1	0	1	0	0	1
1	1	1	0	1	x	0
1	1	1	1	1	x	0

A = S

B = \overline{SR}

 


***5-31.**

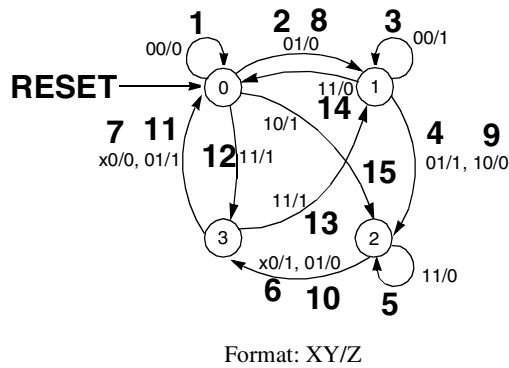


Reset, 00, 01, 00, 01, 11, x0, x0, 01, 10, 01, 01, 11, 11, 11, 10.

5-33.*

 

This simulation was performed without initializing the state of the latches of the flip-flop beforehand. Each gate in the flip-flop implementation has a delay of 1 ns. The interaction of these delays with the input change times produced a narrow pulse in Y at about 55 ns. In this case, the pulse is not harmful since it dies out well before the positive clock edge occurs. Nevertheless, a thorough examination of such a pulse to be sure that it does not represent a design error or important timing problem is critical.

5-37.*

 

Problem Solutions – Chapter 5

5-40.*

```

library IEEE;
use IEEE.std_logic_1164.all;

entity mux_4to1 is
  port (
    S: in STD_LOGIC_VECTOR (1 downto 0);
    D: in STD_LOGIC_VECTOR (3 downto 0);
    Y: out STD_LOGIC
  );
end mux_4to1;
-- (continued in the next column)

architecture mux_4to1_arch of mux_4to1 is
begin
  process (S, D)
  begin
    case S is
      when "00" => Y <= D(0);
      when "01" => Y <= D(1);
      when "10" => Y <= D(2);
      when "11" => Y <= D(3);
      when others => null;
    end case;
  end process;
end mux_4to1_arch;

```

5-45.*

```

library IEEE;
use IEEE.std_logic_1164.all;
entity jkff is
  port (
    J,K,CLK: in STD_LOGIC;
    Q: out STD_LOGIC
  );
end jkff;

architecture jkff_arch of jkff is
  signal q_out: std_logic;
begin

  state_register: process (CLK)
  begin
    if CLK'event and CLK='0' then --CLK falling edge
      -- (continued in the next column)

      case J is
        when '0' =>
          if K = '1' then
            q_out <= '0';
          end if;
        when '1' =>
          if K = '0' then
            q_out <= '1';
          else
            q_out <= not q_out;
          end if;
        when others => null;
      end case;
    end if;
  end process;

  Q <= q_out;
end jkff_arch;

```

5-49.*

```

module problem_6_39 (S, D, Y);

  input [1:0] S;
  input [3:0] D;
  output Y;
  reg Y;

  // (continued in the next column)

  always @(S or D)
  begin
    if (S == 2'b00) Y <= D[0];
    else if (S == 2'b01) Y <= D[1];
    else if (S == 2'b10) Y <= D[2];
    else Y <= D[3];
  end
endmodule

```

5-53.*

```

module JK_FF (J, K, CLK, Q);

  input J, K, CLK;
  output Q;
  reg Q;

  always @(negedge CLK)
  case (J)
    0'b0: Q <= K ? 0: Q;
    1'b1: Q <= K ? ~Q: 1;
  endcase
endmodule

```

