
Solutions to Problems Marked with a * in
Logic and Computer Design Fundamentals, 4th Edition

Chapter 7

© 2008 Pearson Education, Inc.

7-2. *

| | |
|------------------|-----|
| 1001 1001 | |
| <u>1100 0011</u> | |
| 1000 0001 | AND |
| 1101 1011 | OR |
| 0101 1010 | XOR |

7-4. *

sl 1001 0100 sr 0110 0101

7-5. *


Q_i remains connected to MUX data input 0. Connect D_i to MUX data input 1 instead of Mux data input 3. Connect Q_{i-1} to MUX data input 2 instead of MUX data input 1. Finally, 0 is connected to MUX data input 3.

7-6. *

- a) 1000, 0100, 0010, 0001, 1000. ...
- b) # States = n

 7-13.*


The equations given on page 364-5 can be manipulated into SOP form as follows: $D_1 = \overline{Q_1}$, $D_2 = Q_2 \oplus Q_1 \overline{Q_8} = Q_1 \overline{Q_2} \overline{Q_8} + \overline{Q_1} Q_2 + Q_2 Q_8$, $D_4 = Q_4 \oplus Q_1 Q_2 = Q_1 Q_2 \overline{Q_4} + \overline{Q_1} Q_4 + \overline{Q_2} Q_4$, $D_8 = Q_8 \oplus (Q_1 Q_8 + Q_1 Q_2 Q_4) = \overline{Q_8} (Q_1 Q_8 + Q_1 Q_2 Q_4) + Q_8 (\overline{Q_1} + \overline{Q_8}) (\overline{Q_1} + \overline{Q_2} + \overline{Q_4}) = Q_1 Q_2 Q_4 \overline{Q_8} + \overline{Q_1} Q_8$. These equations are mapped onto the K-maps for Table 7-9 below and meet the specifications given by the maps and the table.



To add the enable, change D1 to:

$$D_1 = Q_1 \oplus EN.$$

 For the other three functions, AND EN with the expression XORed with the state variable. The circuit below results.




7-14.*

| Present state | | | Next state | | |
|---------------|---|---|------------|---|---|
| A | B | C | A | B | C |
| 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 | 0 |


a) $D_B = C$ b) $D_A = BC + A\overline{C}$
 $D_C = \overline{B}\overline{C}$ $D_B = \overline{A}\overline{BC} + B\overline{C}$
 $D_C = \overline{C}$

Problem Solutions – Chapter 7


7-17.*

 

7-19.*

 

7-24.*

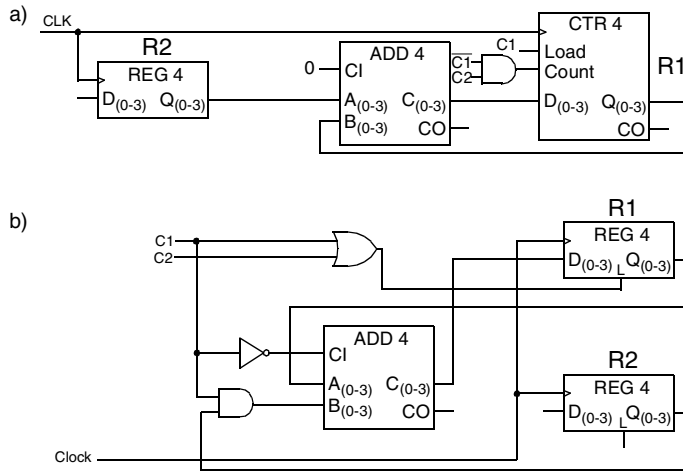


Problem Solutions – Chapter 7

7-27.*

- a) Destination \leftarrow Source Registers b) Source Registers \rightarrow Destination
- | | |
|------------------------|-------------------------|
| R0 \leftarrow R1, R2 | R0 \rightarrow R4 |
| R1 \leftarrow R4 | R1 \rightarrow R0, R3 |
| R2 \leftarrow R3, R4 | R2 \rightarrow R0, R4 |
| R3 \leftarrow R1 | R3 \rightarrow R2 |
| R4 \leftarrow R0, R2 | R4 \rightarrow R1, R2 |

 c) The minimum number of buses needed for operation of the transfers is three since transfer Cb requires three different sources.




7-30.*

0101, 1010, 0101, 1010, 1101, 0110, 0011, 0001, 1000

7-31.*

| Shifts: | 0 | 1 | 2 | 3 | 4 |
|---------|------|------|------|------|------|
| A | 0111 | 0011 | 0001 | 1000 | 1100 |
| B | 0101 | 0010 | 0001 | 0000 | 0000 |
| C | 0 | 1 | 1 | 1 | 0 |


7-32.*

 

7-33.*

State: STA, STA, STB, STC, STA, STB, STC, STA, STB
 Z: 0, 0, 1, 1, 0, 0, 1, 0, -

7-36.*

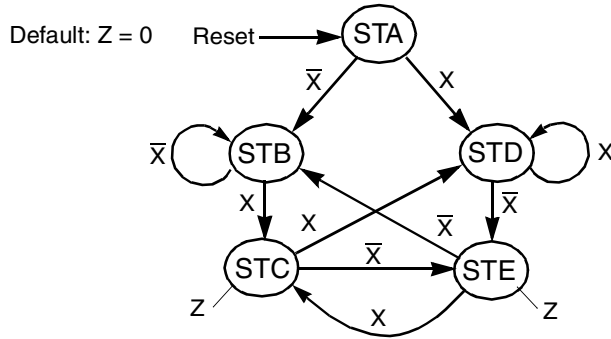

7-39.*

| | Present state | | | Input | Next state | | | Output |
|-----|---------------|---|---|------------------|------------|---|---|--------|
| | A | B | C | | A | B | C | |
| STA | 1 | 0 | 0 | \bar{W} | 1 | 0 | 0 | |
| | 1 | 0 | 0 | W | 0 | 1 | 0 | |
| STB | 0 | 1 | 0 | $\bar{X}Y$ | 1 | 0 | 0 | |
| | 0 | 1 | 0 | X | 0 | 0 | 1 | Z |
| STC | 0 | 0 | 1 | $\bar{X}\bar{Y}$ | 0 | 0 | 1 | Z |
| | 0 | 0 | 1 | | 1 | 0 | 0 | Z |

$$D_A = A\bar{W} + B\bar{X}Y + C$$


$$D_B = AW$$

$$D_C = B(X + \bar{Y})$$


$$Z = B\bar{X}\bar{Y} + C$$


The implementation consists of the logic represented by the above equations and three D flip-flops with Reset connected to S on the first flip-flop and to R on the other two flip-flops.

7-46.*

 

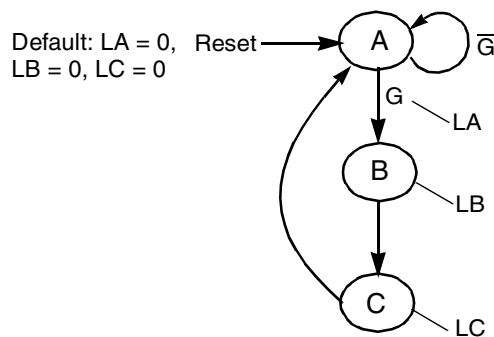R is a synchronous reset that overrides any simultaneous synchronous transfer.



 

7-48.*

```

library IEEE;
use IEEE.std_logic_1164.all;


entity reg_4_bit is
  port (
    CLEAR, CLK: in STD_LOGIC;
    D: in STD_LOGIC_VECTOR (3 downto 0);
    Q: out STD_LOGIC_VECTOR (3 downto 0)
  );
end reg_4_bit;

architecture reg_4_bit_arch of reg_4_bit is
begin

  process (CLK, CLEAR)
  begin
    if CLEAR = '0' then          --asynchronous RESET active Low
      Q <= "0000";
    elsif (CLK'event and CLK='1') then --CLK rising edge
      Q <= D;
    end if;
  end process;

end reg_4_bit_arch;

```

 


7-51.*

```

module register_4_bit (D, CLK, CLR, Q);
input [3:0] D;
input CLK, CLR;
output [3:0] Q;
reg [3:0] Q;

always @(posedge CLK or negedge CLR)
begin
if (~CLR) //asynchronous RESET active low
Q = 4'b0000;
else //use CLK rising edge
Q = D;
end
endmodule

```

 

7-53.*

```

library IEEE;
use IEEE.std_logic_1164.all;
entity prob_7_53 is
port (clk, RESET, W, X, Y : in STD_LOGIC;
Z : out STD_LOGIC);
end prob_7_53;

```

```

architecture process_3 of prob_7_53 is
type state_type is (STA, STB, STC);
signal state, next_state: state_type;
begin

```

```

-- Process 1 - state register
state_register: process (clk, RESET)
begin
if (RESET = '1') then
state <= STA;
else if (CLK'event and CLK='1') then
state <= next_state;
end if;
end if;
end process;

```

```

-- Process 2 - next state function
next_state_func: process (W, X, Y, state)
begin
case state is
when STA =>
-- Continued in next column

```

```

if W = '1' then
next_state <= STB;
else
next_state <= STA;
end if;
when STB =>
if X = '0' and Y = '1' then
next_state <= STA;
else
next_state <= STC;
end if;
when STC =>
next_state <= STA;
end case;
end process;

```

```

-- Process 3 - output function
output_func: process (X, Y, state)
begin
case state is
when STA =>
Z <= '0';
when STB =>
if X = '0' and Y = '0' then
Z <= '1';
else
Z <= '0';
end if;
when STC =>
Z <= '1';
end case;
end process;
end process_3;

```

7-54.*

```

// State Diagram in Figure 5-40 using Verilog
module prob_7_54 (clk, RESET, W, X, Y, Z);
input clk, RESET, W, X, Y;
output Z;

reg[1:0] state, next_state;
parameter STA = 2'b00, STB = 2'b01, STC = 2'b10;
reg Z;

// State Register
always@(posedge clk or posedge RESET)
begin
if (RESET == 1)
state <= STA;
else
state <= next_state;
end

// Next StateFunction
always@(W or X or Y or state)
begin
case (state)
STA: if (W == 1)
next_state <= STB;
else
// (continued in the next column)
next_state <= STA;
STB: if (X == 0 & Y == 1)
next_state <= STA;
else
next_state <= STC;
STC:
next_state <= STA;
endcase
end

// Output Function
always@(X or Y or state)
begin
Z <= 0;
case (state)
STB: if (X == 0 & Y == 0)
Z <= 1;
else
Z <= 0;
STC:
Z <= 1;
endcase
end
endmodule

```