
Logic and Computer Design Fundamentals

Chapter 5 – Sequential Circuits

Part 2 – Sequential Circuit Design

Charles Kime & Thomas Kaminski

© 2008 Pearson Education, Inc.
(Hyperlinks are active in View Show mode)

Overview

- **Part 1 - Storage Elements and Sequential Circuit Analysis**
- **Part 2- Sequential Circuit Design**
 - **Specification**
 - **Formulation**
 - **State Assignment**
 - **Flip-Flop Input and Output Equation Determination**
 - **Verification**
- **Part 3 – State Machine Design**

The Design Procedure

- **Specification**
- **Formulation** - Obtain a state diagram or state table
- **State Assignment** - Assign binary codes to the states
- **Flip-Flop Input Equation Determination** - Select flip-flop types and derive flip-flop equations from next state entries in the table
- **Output Equation Determination** - Derive output equations from output entries in the table
- **Optimization** - Optimize the equations
- **Technology Mapping** - Find circuit from equations and map to flip-flops and gate technology
- **Verification** - Verify correctness of final design

Specification

- **Component Forms of Specification**
 - Written description
 - Mathematical description
 - Hardware description language*
 - Tabular description*
 - Equation description*
 - Diagram describing operation (not just structure)*
- **Relation to Formulation**
 - If a specification is rigorous at the binary level (marked with * above), then all or part of formulation may be completed

Formulation: Finding a State Diagram

- A state is an abstraction of the history of the past applied inputs to the circuit (including power-up reset or system reset).
 - The interpretation of “past inputs” is tied to the synchronous operation of the circuit. E. g., an input value (other than an asynchronous reset) is measured only during the setup-hold time interval for an edge-triggered flip-flop.
- **Examples:**
 - State A represents the fact that a 1 input has occurred among the past inputs.
 - State B represents the fact that a 0 followed by a 1 have occurred as the most recent past two inputs.

Formulation: Finding a State Diagram

- In specifying a circuit, we use states to remember meaningful properties of past input sequences that are essential to predicting future output values.
- A sequence recognizer is a sequential circuit that produces a distinct output value whenever a prescribed pattern of input symbols occur in sequence, i.e., recognizes an input sequence occurrence.
- We will develop a procedure specific to sequence recognizers to convert a problem statement into a state diagram.
- Next, the state diagram, will be converted to a state table from which the circuit will be designed.

Sequence Recognizer Procedure

- To develop a sequence recognizer state diagram:
 - Begin in an initial state in which NONE of the initial portion of the sequence has occurred (typically “reset” state).
 - Add a state that recognizes that the first symbol has occurred.
 - Add states that recognize each successive symbol occurring.
 - The final state represents the input sequence (possibly less the final input value) occurrence.
 - Add state transition arcs which specify what happens when a symbol *not* in the proper sequence has occurred.
 - Add other arcs on non-sequence inputs which transition to states that represent the input subsequence that has occurred.
- The last step is required because the circuit must recognize the input sequence *regardless of where it occurs within the overall sequence applied since “reset.”*

State Assignment

- Each of the m states must be assigned a unique code
- Minimum number of bits required is n such that
$$n \geq \lceil \log_2 m \rceil$$
where $\lceil x \rceil$ is the smallest integer $\geq x$
- There are useful state assignments that use more than the minimum number of bits
- There are $2^n - m$ unused states

Sequence Recognizer Example


- **Example: Recognize the sequence 1101**
 - Note that the sequence 111101 contains 1101 and "11" is a proper sub-sequence of the sequence.
- Thus, the sequential machine must remember that the first two one's have occurred as it receives another symbol.
- Also, the sequence 1101101 contains 1101 as both an initial subsequence and a final subsequence with some overlap, i. e., **1101**101 or 110**1101**.
- And, the 1 in the middle, 1101101, is in both subsequences.
- The sequence 1101 must be recognized each time it occurs in the input sequence.

Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 9

 Example: Recognize 1101

- **Define states for the sequence to be recognized:**
 - assuming it starts with first symbol,
 - continues through each symbol in the sequence to be recognized, and
 - uses output 1 to mean the full sequence has occurred,
 - with output 0 otherwise.
- **Starting in the initial state (Arbitrarily named "A"):**
 - Add a state that recognizes the first "1."
 - State "A" is the initial state, and state "B" is the state which represents the fact that the "first" one in the input subsequence has occurred. The output symbol "0" means that the full recognized sequence has not yet occurred.




Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 10

 
Example: Recognize 1101 (continued)

- After one more 1, we have:

- C is the state obtained when the input sequence has two "1"s.




- Finally, after 110 and a 1, we have:

 


- Transition arcs are used to denote the output function (Mealy Model)
- Output 1 on the arc from D means the sequence has been recognized
- To what state should the arc from state D go? Remember: 1101101 ?
- Note that D is the last state but the output 1 occurs for the input applied in D. This is the case when a *Mealy model* is assumed.


Example: Recognize 1101 (continued)

 

 - Clearly the final 1 in the recognized sequence 1101 is a sub-sequence of 1101. It follows a 0 which is not a sub-sequence of 1101. Thus it should represent *the same state reached from the initial state after a first 1 is observed*. We obtain:



Example: Recognize 1101 (continued)

 


- The state have the following abstract meanings:
 - A: No proper sub-sequence of the sequence has occurred.
 - B: The sub-sequence 1 has occurred.
 - C: The sub-sequence 11 has occurred.
 - D: The sub-sequence 110 has occurred.
 - The 1/1 on the arc from D to B means that the last 1 has occurred and thus, the sequence is recognized.

Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 13

 Example: Recognize 1101 (continued)

- The other arcs are added to each state for inputs not yet listed. Which arcs are missing?




- Answer:
 - "0" arc from A
 - "0" arc from B
 - "1" arc from C
 - "0" arc from D.

Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 14

 Example: Recognize 1101 (continued)


- State transition arcs must represent the fact that an input subsequence has occurred. Thus we get:



- Note that the 1 arc from state C to state C implies that State C means *two or more 1's have occurred*.

Formulation: Find State Table

 
- From the State Diagram, we can fill in the State Table.
- There are 4 states, one input, and one output. We will choose the form with four rows, one for each current state.
- From State A, the 0 and 1 input transitions have been filled in along with the outputs.



Present State	Next State		Output	
	x=0	x=1	x=0	x=1
A	A	B	0	0
B				
C				
D				

Formulation: Find State Table

 - From the state diagram, we complete the state table.



Present State	Next State		Output	
	x=0	x=1	x=0	x=1
A	A	B	0	0
B	A	C	0	0
C	D	C	0	0
D	A	B	0	1

- What would the state diagram and state table look like for the Moore model?

Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 17

Example: Moore Model for Sequence 1101


- For the Moore Model, outputs are associated with states.
- We need to add a state "E" with output value 1 for the final 1 in the recognized input sequence.
 - This new state E, though similar to B, would generate an output of 1 and thus be different from B.
- The Moore model for a sequence recognizer usually has *more states* than the Mealy model.

Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 18

 Example: Moore Model (continued)

- We mark outputs on states for Moore model
- Arcs now show only state transitions
- Add a new state E to produce the output 1
- Note that the new state, E produces the same behavior in the future as state B. But it gives a different output at the present time. Thus these states do represent a *different abstraction* of the input history.




Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 19

 Example: Moore Model (continued)

- The state table is shown below
- Memory aid re more state in the Moore model: “Moore is More.”



Present State	Next State		Output y
	x=0	x=1	
A	A	B	0
B	A	C	0
C	D	C	0
D	A	E	0
E	A	C	1

Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 20

State Assignment – Example 1

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
A	A	B	0	0
B	A	B	0	1

- **How many assignments of codes with a minimum number of bits?**
 - Two – A = 0, B = 1 or A = 1, B = 0
- **Does it make a difference?**
 - Only in variable inversion, so small, if any.

State Assignment – Example 2

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
A	A	B	0	0
B	A	C	0	0
C	D	C	0	0
D	A	B	0	1

- **How many assignments of codes with a minimum number of bits?**
 - $4 \times 3 \times 2 \times 1 = 24$
- **Does code assignment make a difference in cost?**

State Assignment – Example 2 (continued)

- **Counting Order Assignment: A = 0 0, B = 0 1, C = 1 0, D = 1 1**
- **The resulting coded state table:**

Present State	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
0 0	0 0	0 1	0	0
0 1	0 0	1 0	0	0
1 0	1 1	1 0	0	0
1 1	0 0	0 1	0	1

Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 23

State Assignment – Example 2 (continued)

- **Gray Code Assignment: A = 0 0, B = 0 1, C = 1 1, D = 1 0**
- **The resulting coded state table:**

Present State	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
0 0	0 0	0 1	0	0
0 1	0 0	1 1	0	0
1 1	1 0	1 1	0	0
1 0	0 0	0 1	0	1

Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 24

Find Flip-Flop Input and Output Equations: Example 2 – Counting Order Assignment

- Assume D flip-flops
- Interchange the bottom two rows of the state table, to obtain K-maps for D_1 , D_2 , and Z :

D_1		X		
	0	0		
	0	1		
Y_1	0	0		Y_2
	1	1		

D_2		X		
	0	1		
	0	0		
Y_1	0	1		Y_2
	1	0		

Z		X		
	0	0		
	0	0		
Y_1	0	0		Y_2
	0	1		

Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 25

Optimization: Example 2: Counting Order Assignment

- Performing two-level optimization:

D_1		X		
	0	0		
	0	1		
Y_1	0	0		Y_2
	1	1		

D_2		X		
	0	1		
	0	0		
Y_1	0	1		Y_2
	1	0		

Z		X		
	0	0		
	0	0		
Y_1	0	0		Y_2
	0	1		

$$D_1 = Y_1 \bar{Y}_2 + X \bar{Y}_1 Y_2$$

$$D_2 = \bar{X} Y_1 \bar{Y}_2 + X \bar{Y}_1 \bar{Y}_2 + X Y_1 Y_2$$

$$Z = X Y_1 \bar{Y}_2$$

Gate Input Cost = 22

Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 26

Find Flip-Flop Input and Output Equations: Example 2 – Gray Code Assignment

- Assume D flip-flops
- Obtain K-maps for D_1 , D_2 , and Z :

D_1		X	
		0	0
		0	1
Y_1		1	1
		0	0

D_2		X	
		0	1
		0	1
Y_1		0	1
		0	1

Z		X	
		0	0
		0	0
Y_1		0	0
		0	1

Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 27

Optimization: Example 2: Assignment 2

- Performing two-level optimization:

D_1		X	
		0	0
		0	1
Y_1		1	1
		0	0

D_2		X	
		0	1
		0	1
Y_1		0	1
		0	1

Z		X	
		0	0
		0	0
Y_1		0	0
		0	1

$$D_1 = Y_1 Y_2 + X \bar{Y}_2$$

Gate Input Cost = 9

$$D_2 = X$$

Select this state assignment to

$$Z = X Y_1 \bar{Y}_2$$

complete design in slide

Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 28

One Flip-flop per State (One-Hot) Assignment

- Example codes for four states: $(Y_3, Y_2, Y_1, Y_0) = 0001, 0010, 0100, \text{ and } 1000$.
- In equations, need to include only the variable that is 1 for the state, e. g., state with code 0001, is represented in equations by Y_0 instead of $\overline{Y_3} \overline{Y_2} \overline{Y_1} Y_0$ because all codes with 0 or two or more 1s have don't care next state values.
- Provides simplified analysis and design
- Combinational logic may be simpler, but flip-flop cost higher – may or may not be lower cost

State Assignment – Example 2 (continued)

- One-Hot Assignment : A = 0001, B = 0010, C = 0100, D = 1000 The resulting coded state table:

Present State	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
0001	0001	0010	0	0
0010	0001	0100	0	0
0100	1000	0100	0	0
1000	0001	0010	0	1

Optimization: Example 2: One Hot Assignment

- Equations read from 1 next state variable entries in table:

$$D_0 = X(Y_0 + Y_1 + Y_3) \text{ or } X \bar{Y}_2$$

$$D_1 = \bar{X}(Y_0 + Y_3)$$

$$D_2 = X(Y_1 + Y_2) \text{ or } X(\bar{Y}_0 + \bar{Y}_3)$$

$$D_3 = \bar{X} Y_2$$

$$Z = XY_3 \text{ Gate Input Cost} = 15$$

- Combinational cost intermediate plus cost of two more flip-flops needed.


Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 31

Map Technology

- Library:
- Initial Circuit:

 
- D Flip-flops with Reset (not inverted)
- NAND gates with up to 4 inputs and inverters



Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 32

Mapped Circuit - Final Result

 

Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 33

Sequential Design: Example 3


- Design a sequential modulo 3 accumulator for 2-bit operands
- Definitions:
 - Modulo n adder - an adder that gives the result of the addition as the remainder of the sum divided by n
 - Example: $2 + 2$ modulo 3 = remainder of $4/3 = 1$
 - Accumulator - a circuit that “accumulates” the sum of its input operands over time - it adds each input operand to the stored sum, which is initially 0.
- Stored sum: (Y_1, Y_0) , Input: (X_1, X_0) , Output: (Z_1, Z_0)

Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 34

Example 3 (continued)

- Complete the state diagram:

 

Example 3 (continued)


- Complete the state table

X_1X_0 Y_1Y_0	00	01	11	10	Z_1Z_0
	$Y_1(t+1),$ $Y_0(t+1)$	$Y_1(t+1),$ $Y_0(t+1)$	$Y_1(t+1),$ $Y_0(t+1)$	$Y_1(t+1),$ $Y_0(t+1)$	
A (00)	00		X		00
B (01)			X		01
- (11)	X	X	X	X	11
C (10)			X		10

- State Assignment: $(Y_1, Y_0) = (Z_1, Z_0)$
- Codes are in gray code order to ease use of K-maps in the next step

 Example 3 (continued)

- Find optimized flip-flop input equations for D flip-flops




- $D_1 =$
- $D_0 =$

Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 37

Circuit - Final Result with AND, OR, NOT

 

Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 38

Other Flip-Flop Types

- **J-K and T flip-flops**
 - Behavior
 - Implementation
- **Basic descriptors for understanding and using different flip-flop types**
 - Characteristic tables
 - Characteristic equations
 - Excitation tables
- **For actual use, see Reading Supplement - Design and Analysis Using J-K and T Flip-Flops**

Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 39

J-K Flip-flop

- **Behavior**
 - Same as S-R flip-flop with J analogous to S and K analogous to R
 - Except that $J = K = 1$ is allowed, and
 - For $J = K = 1$, the flip-flop changes to the *opposite state*
 - As a master-slave, has same “1s catching” behavior as S-R flip-flop
 - If the master changes to the wrong state, that state will be passed to the slave
 - E.g., if master falsely set by $J = 1, K = 1$ cannot reset it during the current clock cycle


Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 40


J-K Flip-flop (continued)

Implementation

 - To avoid 1s catching behavior, one solution used is to use an edge-triggered D as the core of the flip-flop



Symbol

 

Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 41

T Flip-flop

Behavior

- Has a single input T
 - For $T = 0$, no change to state
 - For $T = 1$, changes to opposite state
- Same as a J-K flip-flop with $J = K = T$
- As a master-slave, has same “1s catching” behavior as J-K flip-flop
- Cannot be initialized to a known state using the T input
 - Reset (asynchronous or synchronous) essential


Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 42


T Flip-flop (continued)

Implementation

 - To avoid 1s catching behavior, one solution used is to use an edge-triggered D as the core of the flip-flop



Symbol

 

Basic Flip-Flop Descriptors

Used in analysis

- Characteristic table** - defines the next state of the flip-flop in terms of flip-flop inputs and current state
- Characteristic equation** - defines the next state of the flip-flop as a Boolean function of the flip-flop inputs and the current state

Used in design

- Excitation table** - defines the flip-flop input variable values as function of the current state and next state

D Flip-Flop Descriptors

- **Characteristic Table**

D	Q(t+1)	Operation
0	0	Reset
1	1	Set

- **Characteristic Equation**

$$Q(t+1) = D$$

- **Excitation Table**

Q(t+1)	D	Operation
0	0	Reset
1	1	Set

T Flip-Flop Descriptors

- **Characteristic Table**

T	Q(t+1)	Operation
0	$Q(t)$	No change
1	$\bar{Q}(t)$	Complement

- **Characteristic Equation**

$$Q(t+1) = T \oplus Q$$

- **Excitation Table**

Q(t+1)	T	Operation
$Q(t)$	0	No change
$\bar{Q}(t)$	1	Complement

S-R Flip-Flop Descriptors

- Characteristic Table

S	R	Q(t+1)	Operation
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	?	Undefined

- Characteristic Equation

$$Q(t+1) = S + \bar{R} Q, S \cdot R = 0$$

- Excitation Table

Q(t)	Q(t+1)	S	R	Operation
0	0	0	X	No change
0	1	1	0	Set
1	0	0	1	Reset
1	1	X	0	No change

Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 47

J-K Flip-Flop Descriptors

- Characteristic Table

J	K	Q(t+1)	Operation
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$\bar{Q}(t)$	Complement

- Characteristic Equation

$$Q(t+1) = J \bar{Q} + \bar{K} Q$$

- Excitation Table


Q(t)	Q(t+1)	J	K	Operation
0	0	0	X	No change
0	1	1	X	Set
1	0	X	1	Reset
1	1	X	0	No Change

Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 48

Flip-flop Behavior Example

 - Use the characteristic tables to find the output waveforms for the flip-flops shown:




Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 49

Flip-Flop Behavior Example (continued)

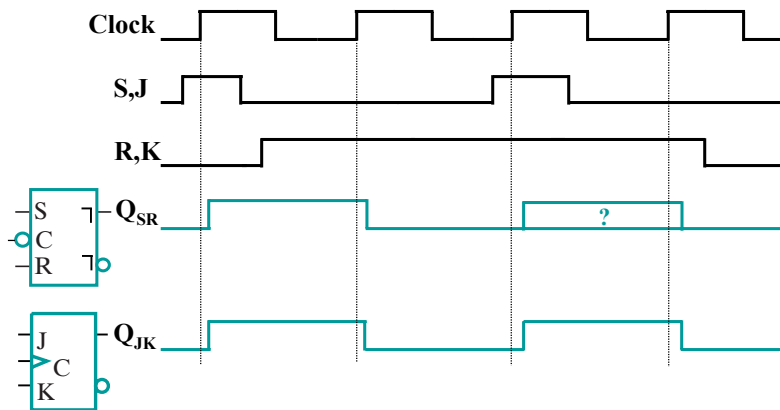- Use the characteristic tables to find the output waveforms for the flip-flops shown:



Logic and Computer Design Fundamentals, 4e
PowerPoint® Slides
© 2008 Pearson Education, Inc.

Chapter 5 - Part 2 50

Terms of Use

- **All (or portions) of this material © 2008 by Pearson Education, Inc.**
- **Permission is given to incorporate this material or adaptations thereof into classroom presentations and handouts to instructors in courses adopting the latest edition of Logic and Computer Design Fundamentals as the course textbook.**
- **These materials or adaptations thereof are not to be sold or otherwise offered for consideration.**
- **This Terms of Use slide or page is to be included within the original materials or any adaptations thereof.**