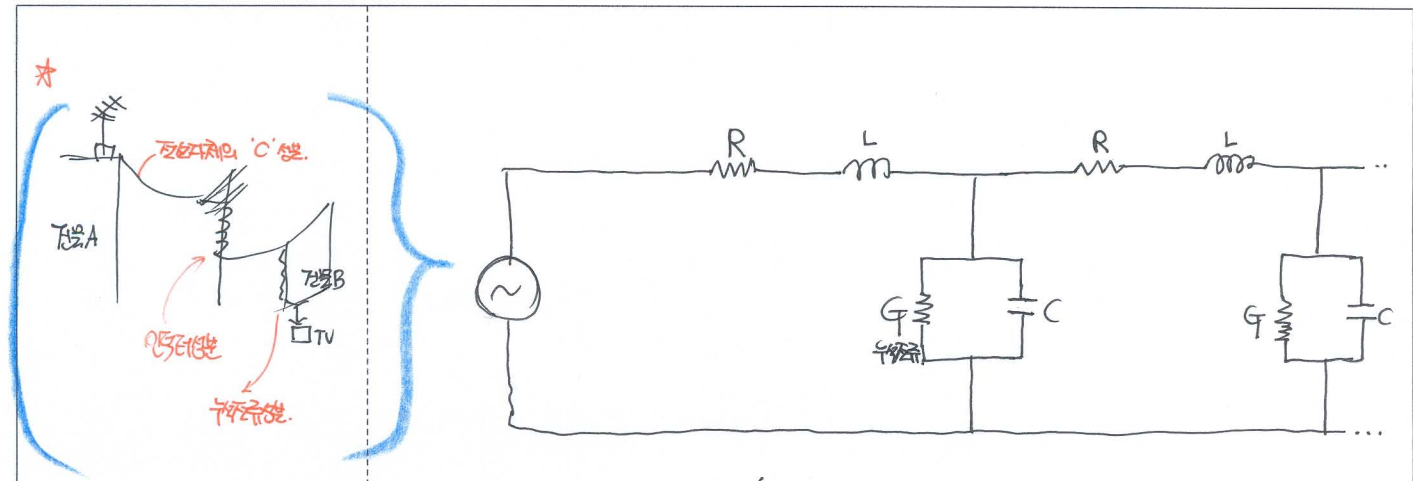


$$\begin{cases} R & \Omega/\text{m} \\ L & \text{H}/\text{m} \\ G & \text{S}/\text{m} \\ C & \text{F}/\text{m} \end{cases}$$

$$\frac{dV(z)}{dz} = -I(z) \cdot Z$$

$$\frac{dI(z)}{dz} = -V(z) \cdot Y$$

where, $Z = R + j\omega L = R + j\omega L$
 $Y = G + j\omega C = G + j\omega C$

$$\frac{d^2 V(z)}{dz^2} = r^2 V(z)$$

$$\text{where, } r^2 = Z \cdot Y$$

$$\frac{d^2 I(z)}{dz^2} = r^2 I(z)$$

$$r = \sqrt{(R + j\omega L)(G + j\omega C)}$$

전파상수
propagation Constant

$$= \text{Real} + j \text{Imaginary}$$

$$= \alpha + j\beta$$

$$\left\{ \begin{array}{l} \frac{G}{C} = \sigma / \epsilon \\ LC = \mu \epsilon \\ \downarrow \\ \text{두께} \end{array} \right.$$

→ 값을 알 수 있다.

< Chong 책 383p > *

1) 평판 전송 선 (parallel - plate transmission line)

$$C = \epsilon S/d \quad \left\{ \begin{array}{l} \text{폭} \quad W \\ \text{두께} \quad d. \end{array} \right. \quad (\epsilon, \mu \text{ 파라미터})$$

$$C = \epsilon S/d \approx \text{이름} \rightarrow$$

$$\left\{ \begin{array}{l} C = \epsilon \frac{W}{d} \quad [F/m] \\ L = \mu \frac{\epsilon}{C} = \mu \frac{W}{d} \quad [H/m] \\ G = \sigma / \epsilon \cdot C = \sigma \cdot \frac{W}{d} \quad [S/m] \end{array} \right.$$

* $LC = \mu \epsilon$

$$\frac{G}{C} = \sigma / \epsilon$$

- 단위 길이당 R .

$$R = \frac{l}{\sigma_c \cdot S}$$

$\overset{\text{길이}}{l}$ $\underset{\text{표면적}}{S}$ 공식으로부터.

chay 문제 9장 참고.

$$= \frac{1}{\sigma_c \cdot (\omega \cdot \delta)}$$

$$\delta: \text{표면적} = 1/\alpha = 1/\sqrt{\pi \mu f \sigma}$$

두 평행판에서 (정제)

$$R = \frac{2l}{\sigma_c \cdot \omega \cdot \delta}$$


$$= \frac{2}{\omega} \cdot \sqrt{\frac{\pi f \mu_c}{\sigma_c}} \quad [\Omega/m]$$

$$\text{주파수} \uparrow \propto R \uparrow$$

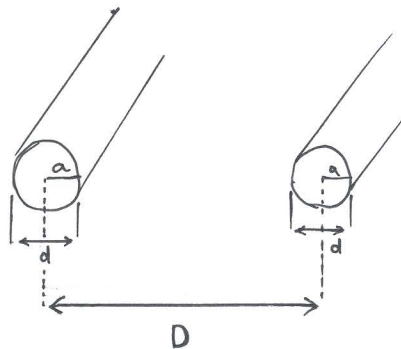2) Two - Wire (2선 전송 선로) Transmission Line.

: 반경이 각각 a 인 두개의 도선이 유전체 매질 (ϵ, μ) 에서
거리 D 만큼 떨어져 있는 경우.

$$\begin{cases} LC = \mu\epsilon \\ G/C = \sigma/\epsilon \end{cases}$$



$$C = \frac{\pi\epsilon}{\cosh^{-1}(D/2a)} \quad [F/m]$$

$$L = \frac{\mu}{\pi} \cdot \cosh^{-1}\left(\frac{D}{2a}\right) \quad [H/m]$$


$$G = \frac{\pi\sigma}{\cosh^{-1}(D/2a)}$$

$$R = \frac{l}{\sigma S} = \frac{l}{\sigma(\pi a s)} \quad [R = \Omega/m]$$

or

$$\frac{1}{\pi a} \sqrt{\frac{\pi f \mu_c}{\sigma_c}}$$

동축 케이블 (coaxial transmission line)

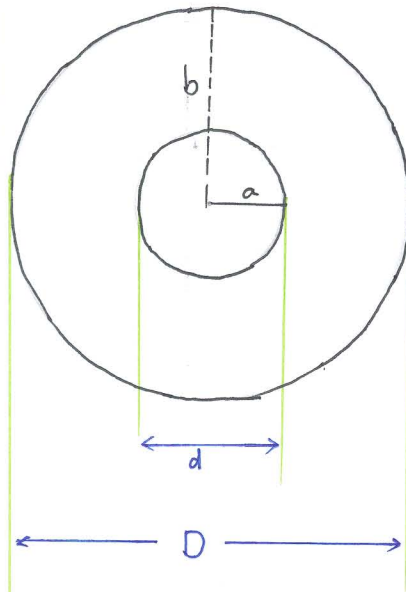

$$* \begin{cases} d = 2a \\ D = 2b \end{cases}$$

$$C = Q/V \text{ V.}$$

$$= \frac{2\pi\epsilon}{\ln(b/a)}$$

$$L = \frac{\mu}{2\pi} \ln\left(\frac{b}{a}\right)$$

$$G = \frac{2\pi\sigma}{\ln\left(\frac{b}{a}\right)} \quad [S/m]$$

$$R = \frac{l}{\sigma \cdot S_{inner}} + \frac{l}{\sigma \cdot S_{out}}$$

$\swarrow$ $\swarrow$
 내부 전선 단면적 외부 전선 단면적

$$* \begin{cases} S_{inner} = 2\pi a l \\ S_{out} = 2\pi b l \end{cases}$$

$$= \frac{l}{2\pi\sigma} \left(\frac{1}{a} + \frac{1}{b} \right)$$

or.

$$R = \frac{l}{2\pi} \left(\frac{1}{a} + \frac{1}{b} \right) \sqrt{\frac{\pi f \mu}{\sigma}} \quad (f: \text{주파수})$$

* Infinite trans. Line (무한장 전송 선.)

* 문제 7p - A(2)

A(2)에서 $V(z)$, $I(z)$ 를 구하면

$$\begin{cases} \frac{d^2 V}{dz^2} = r^2 V(z) \\ \frac{d^2 I}{dz^2} = r^2 I(z) \end{cases}$$

특정해인 해 e^{-rz} , e^{rz}

$$\therefore V(z) = V_0^+ e^{-rz} + V_0^- e^{+rz} \quad \text{) (7) A.}$$

$$I(z) = I_0^+ e^{-rz} + I_0^- e^{+rz}$$

→ 전송 선의 전류·전압 방정식.

* A(1)

$$(1) \begin{cases} \frac{dV(z)}{dz} = -Z \cdot I(z) \\ \frac{dI(z)}{dz} = -Y \cdot V(z) \end{cases}$$

A(1) → A(1)에 대입

$$\frac{d(V_0^+ e^{-rz} + V_0^- e^{rz})}{dz} = -I(z) \cdot Z$$

$$-r V_0^+ e^{-rz} + r V_0^- e^{rz} = -I(z) \cdot Z$$

$$\therefore I(z) = \frac{r(V_0^+ e^{-rz} - V_0^- e^{rz})}{Z} = \frac{r}{Z} (V_0^+ e^{-rz} - V_0^- e^{rz})$$

* where, $\frac{r}{Z} = \frac{\sqrt{Z \cdot Y}}{Z} = \sqrt{\frac{Y}{Z}} = \frac{1}{Z_c} = \frac{1}{Z_0}$
특성 임피던스.

$$\left(\begin{array}{l} V = V_0^+ e^{-rZ} + V_0^- e^{rZ} \\ I = I_0^+ e^{-rZ} + I_0^- e^{rZ} \end{array} \right)$$

where, $Z_c, Z_0 = \sqrt{\frac{Z}{Y}}$
 "Characteristic Impedance of Line."
 $= \sqrt{\frac{R + j\omega L}{G + j\omega C}}$

$\Rightarrow$

• 매우 낮은 주파수에서 $Z_0 = \sqrt{\frac{R}{G}}$.


• 매우 높은 주파수에서 $Z_0 = \sqrt{\frac{L}{C}}$

무선 $R=G=\alpha=0$

* $r = \alpha + j\beta$
 $\downarrow$
 감쇠계수.

$R \ll j\omega L$

$G \ll j\omega C$

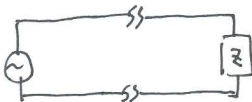

$$I(z) = \frac{1}{Z_0} \left(\underbrace{V_0^+ e^{-rZ}}_{V_1} - \underbrace{V_0^- e^{rZ}}_{V_2} \right)$$

If 1) $Z \rightarrow \infty$ (선로의 끝이 매우 길다. 무한 길이)

$e^{rZ} \rightarrow \infty$ 지어 $V_2 = 0$ 이어야 함.

$\therefore I(z) = \frac{1}{Z_0}$

$$\begin{aligned} \therefore V(z) &= V_0^+ e^{-\gamma z} \\ I(z) &= \frac{V_0^+}{Z_0} e^{-\gamma z} \end{aligned} \left. \vphantom{\begin{aligned} \therefore V(z) &= V_0^+ e^{-\gamma z} \\ I(z) &= \frac{V_0^+}{Z_0} e^{-\gamma z} \end{aligned}} \right\} \begin{array}{l} \text{무한장 선로에서} \\ \text{전류 전압 방정식} \end{array}$$